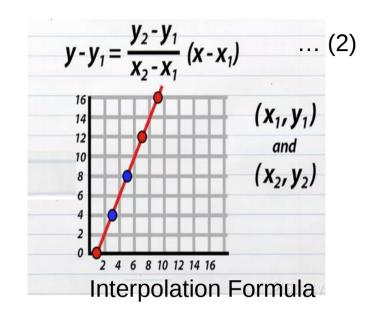
## Feb-25-2019 Compensation Function for ADC

$$f(x) + g(x) = ax + b$$
 ... (1)

Where ax + b is the ideal linear characteristics of the ADC, f(x) is the actual ADC function (piece wise linear), and g(x) is the compensation function to be designed. Note b = 0, and a is a slop for the ADC, for 10 bits ADC, a = 1024/3.3, f(x) is from the ADC data characteristic curve and g(x) is the compensation function to be designed.



So 
$$f(x) + g(x) = ax$$
 and

Based on equation (2), we can write f(x) as

$$f(x) = px + q$$
 ... (3)

p and q can be found from the actual experiment. Substitute eqn(3) back to (1),

we have


$$px + q + g(x) = ax$$
  
 $px + q + a_g x + b_g = ax$ 

Therefore:

$$b_g = -q; a_g = (a - p)$$
 ... (4)

### Feb-25-2019 ADC Compensation Example

## A/D Converter

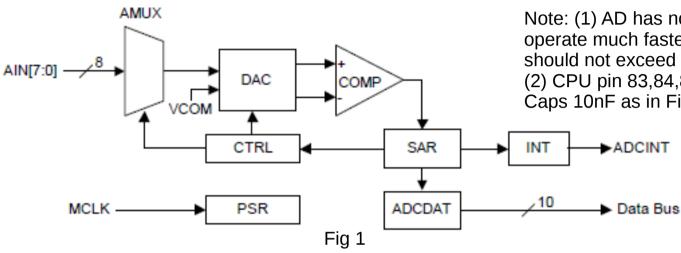

Note: (1) AD has no built-in S/H circuit. Even it can operate much faster, but without S/H, the sampling speed should not exceed 100 Hz;

(2) CPU pin 83,84,85 must have external compensation Caps 10nF as in Fig 2;

(3) Problem 1 of the ADC: ADCCON's ADC state flag off by 1 right after the conversion starts and right before the conversion ends;

	PSR	Prescaler register: define sample speed		
	ADCCON	ADC control register		
	ADCDAT	ADC data register		
	SAR	Successive approximation register $CLK_{CPU}$	1/ f	
1	Conv =	(1) Conv -	L/ Conv	(2)
	2	* (N <sub>PSR</sub> + 1)		

(4) Problem 2 of the ADC: No S/H therefore ADC error can be large, need to reduce the output impedance of the analog signal source.

Example: For a given signal, we have  $f_{Sampling} = 98.2$  KHz, find  $N_{PSR}$  to realize this AD design requirement. Ans:  $N_{PSR} = 20$ 

# ADC Theoretical Background


ADC voltage resolution Q calculation

$$Q = \frac{E_{FSR}}{N}$$

Where 
$$E_{FSR} = V_{R,High} - V_{R,Low}$$
  
and  $N = 2^{X}$ 
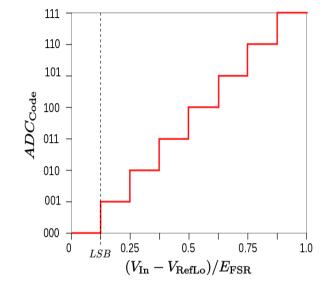
#### Example 1

- \* Coding scheme as in figure 3
- \* Full scale measurement range = 0 to 10 volts
- \* ADC resolution is 12 bits: 212 = 4096 quantization levels (codes)
- \* ADC voltage resolution, Q = (10V 0V) / 4096 = 10V / 4096 \approx 0.00244 V \approx 2.44 mV.




http://en.wikipedia.org/wiki/File:ADC\_voltage\_r esolution.svg

Fig 3

DFT (FFT: fast Fourier Transform) based AD conversion validation.

## **ADC Characterization**

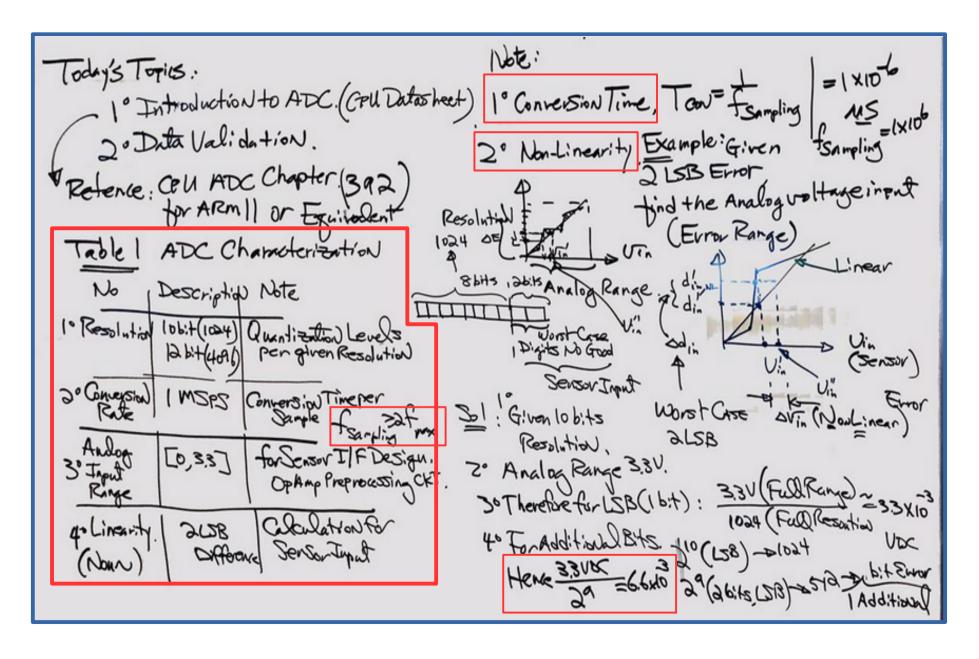

## Introduction To DFT For Data Validation

